# Assignment 7

#### Giridhar Paida

January 2021

## 1 Question

For any two statements p and q the negation of expression p  $\bigvee$  ( p  $\bigwedge$  q) is:

- 1.  $\sim p \wedge \sim q$
- 2. p ∧ q
- 3.  $p \leftrightarrow q$
- 4. ~p ∨ ~q

The correct answer is (1).

### 2 Boolean Expression

$$F = \overline{p} \,\overline{q} \tag{1}$$

## 3 Circuit Diagram

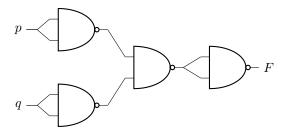


Figure 1: Logic gates